

BINARY CODED DECIMAL: **B.C.D.**

- ANOTHER METHOD TO REPRESENT DECIMAL NUMBERS
- USEFUL BECAUSE MANY DIGITAL DEVICES PROCESS + DISPLAY NUMBERS IN TENS

IN **BCD EACH** NUMBER IS DEFINED BY A BINARY CODE OF **4 BITS**.

***** 8 – 4 – 2 – 1** MOST COMMON CODE

8 – 4 – 2 – 1 CODE INDICATES THE WEIGHT OF EACH BIT $2^3 - 2^2 - 2^1 - 2^0$

E.G. 934 = 1001 0011 0100
 9 3 4

FOR **EACH** DIGIT A **BINARY** [NORMAL] **CODE** IS ALLOCATED.

OTHER REPRESENTATION FORMS ARE **2-4-2-1** AND **EXCESS-3**

BINARY	8-4-2-1	2-4-2-1	EXCESS-3
0000	0	0	NOT USED
0001	1	1	NOT USED
0010	2	2	NOT USED
0011	3	3	0
0100	4	4	1
0101	5	NOT USED	2
0110	6	NOT USED	3
0111	7	NOT USED	4
1000	8	NOT USED	5
1001	9	NOT USED	6
1010	NOT USED	NOT USED	7
1011	NOT USED	5	8
1100	NOT USED	6	9
1101	NOT USED	7	NOT USED
1110	NOT USED	8	NOT USED
1111	NOT USED	9	NOT USED

- WE WILL USE 8-4-2-1 BCD
- DECIMAL NUMBERS > 9 MAY BE OBTAINED WHEN ADDING TWO DECIMAL DIGITS (RANGE: 0-18) I.E. $0 + 0 \div 9 + 9$. ONLY 0→9 HAVE THE CORRECT BCD CODE.
- WE NEED TO CORRECT THE OTHERS

DECIMAL	UNCORRECTED					CORRECTED				
	BCD SUM					BCD SUM				
	C'_3	S'_3	S'_2	S'_1	S'_0	C_N	S_3	S_2	S_1	S_0
0	0	0	0	0	0	0	0	0	0	0
⋮		⋮					⋮			
9	1	0	0	1		1	0	0	1	
10	1	0	1	0		1	0	0	0	0
11	1	0	1	1		1	0	0	0	1
12	1	1	0	0		1	0	0	1	0
13	1	1	0	1		1	0	0	1	1
14	1	1	1	0		1	0	1	0	0
15	1	1	1	1		1	0	1	0	1
16	1	0	0	0	0	1	0	1	1	0
17	1	0	0	0	1	1	0	1	1	1
18	1	0	0	1	0	1	1	0	0	0
19	1	0	0	1	1	1	1	0	0	1

- **0→9 ONLY LEGAL CODES**

E.G. 19 = 1 9 = 0001 1001 = 11001

THUS, FOR SUMS BETWEEN 10 → 18 MUST SUBTRACT 10 AND PRODUCE A CARRY

SUBTRACT 10 = 1010₂ >> ADD 2's COMPLEMENT = 0110

4-BIT BCD ADDER

TO ADD TWO DIGITS

FOR SUMS >9 WE NEED TO ADD 2's COMPLEMENT of 10_{10} TO THE UNCORRECTED RESULT ($S'_3 S'_2 S'_1 S'_0$)

CORRECTION IS ALSO NEEDED WHEN A CARRY OUT (C'_3) IS GENERATED [NUMBERS 16 \rightarrow 18]

>>>> A DECODER IS REQUIRED TO DETECT WHEN CARRY OUT (C_N) TO THE NEXT STAGE IS NEEDED

K-MAP FOR C_N

		$S'_1 S'_0$			
		00	01	11	10
$S'_3 S'_2$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

>>>> $C_N = C'_3 + S'_3 S'_2 + S'_3 S'_1$

BCD SUBTRACTION

9's COMPLEMENT

THE **9's COMPLEMENT** OF A **DECIMAL NUMBER** IS FOUND BY **SUBTRACTING EACH DIGIT** IN THE NUMBER FROM **9**

DECIMAL DIGIT	9's COMPLEMENT
0	9
1	8
2	7
⋮	⋮
9	0

$$\text{E.G. } 9's \text{ COMPLEMENT of } 28 = 99 - 28 \\ = 71$$

$$9's \text{ COMPLEMENT of } 562 = 999 - 562 \\ = 437$$

SUBTRACTION OF A SMALLER DECIMAL NUMBER FROM A LARGER ONE CAN BE DONE BY ADDING THE 9's COMPLEMENT OF THE SMALLER NUMBER TO THE LARGER NUMBER AND THEN ADDING THE CARRY TO THE RESULT (END AROUND CARRY).

WHEN SUBTRACTING A LARGER NUMBER FROM A SMALLER ONE THERE IS NO CARRY AND THE RESULT IS IN 9's COMPLEMENT FORM AND NEGATIVE.

EXAMPLES:

(a)
$$\begin{array}{r} +8 \\ -3 \\ \hline 5 \end{array}$$

$$\begin{array}{r} +8 \\ +6 \leftarrow \text{9's COMP. OF 3} \\ \hline (1) 4 \\ +1 \quad \text{END AROUND CARRY} \\ \hline 5 \end{array}$$

(b)
$$\begin{array}{r} 54 \\ -21 \\ \hline 33 \end{array}$$

$$\begin{array}{r} 54 \\ 78 \leftarrow \text{9's COMP. OF 3} \\ \hline (1) 32 \\ +1 \quad \text{END AROUND CARRY} \\ \hline 33 \end{array}$$

(c)
$$\begin{array}{r} 15 \\ -28 \\ \hline -13 \end{array}$$

$$\begin{array}{r} 15 \\ +71 \leftarrow \text{9's COMP. OF 3} \\ \hline 86 \rightarrow -13 \end{array}$$

NO CARRY >>> NEGATIVE RESULT

$86 - 99 = -13$

BCD SUBTRACTION

RECALL FOR DECIMAL SUBTRACTION:

$$A - B = A + [9\text{'s COMPLEMENT OF } B]$$

- **SIMILARLY FOR BCD**

RULES:

- ADD 9's COMP. OF B TO A**
- IF RESULT > 9, CORRECT BY
ADDING 0110**
- IF MOST SIGNIFICANT CARRY
IS PRODUCED [i.e. =1] THEN
THE RESULT IS POSITIVE AND
THE END AROUND CARRY MUST
BE ADDED.**
- IF MOST SIGNIFICANT CARRY
IS 0 [i.e. NO CARRY] THEN THE
RESULT IS NEGATIVE AND WE
GET THE 9's COMP. OF THE RESULT**

E.G. $8 - 3 = 8 + [9\text{'s COMP. OF } 3]$
 $= 8 + 6$

$$\begin{array}{r}
 1000 \\
 \underline{0110} \\
 1110 \quad \leftarrow \text{INVALID } (>9) \\
 \underline{0110} \quad \leftarrow \text{CORRECTION} \\
 (1) \ 0100 \\
 \quad \leftarrow \underline{1} \quad \leftarrow \text{END AROUND CARRY} \\
 \quad \underline{0101} = 5
 \end{array}$$

(b) $3 - 8 = -5$

$$\begin{array}{r}
 0011 \\
 \underline{0001} \\
 0100
 \end{array}$$

NO CARRY >>> NEGATIVE
9's COMP. OF 0100 = 0101 = -5

(c) $87 - 39 >>> 87 + [9\text{'s COMP OF } 39]$

$$\begin{array}{r}
 87 \quad 1000 \quad 0111 \\
 60 \quad \underline{0110} \quad \underline{0000} \\
 \quad \leftarrow 1110 \quad 0111 \\
 \text{INVALID} \quad \underline{0110} \\
 \quad (1) \ 0100 \quad 0111 \\
 \quad \quad \leftarrow \underline{1} \\
 \quad \quad \underline{0100} \quad \underline{1000} \\
 = \quad \quad \mathbf{4} \quad \quad \mathbf{8}
 \end{array}$$


(d) $18 - 72 \ggg 18 + [27]$

0001	1000	
0010	0111	
0011	1111	→ NO CARRY NEGATIVE
0001	0110	↙ ↘
0100	(1) 0101	CORRECTION
4	5 = -54	

OUTPUT IS A **NEGATIVE** NUMBER >>
 THE RESULT IS IN **9's COMP.** FORM

(e) $65 - 12 \ggg 65 + [87]$

0110	0101									
1000	0111									
1110	1100	→ INVALID								
0110	0110	CORRECTION								
(1) 0100	(1) 0010									
<table style="border-collapse: collapse; margin: 0 auto;"> <tr> <td style="padding: 5px;">1</td> <td style="padding: 5px;">←</td> </tr> <tr> <td style="border-top: 1px solid black; padding: 5px;">0101</td> <td></td> </tr> </table>	1	←	0101		<table style="border-collapse: collapse; margin: 0 auto;"> <tr> <td style="padding: 5px;">1</td> <td style="padding: 5px;">←</td> </tr> <tr> <td style="border-top: 1px solid black; padding: 5px;">0011</td> <td></td> </tr> </table>	1	←	0011		END AROUND CARRY
1	←									
0101										
1	←									
0011										
5	3									

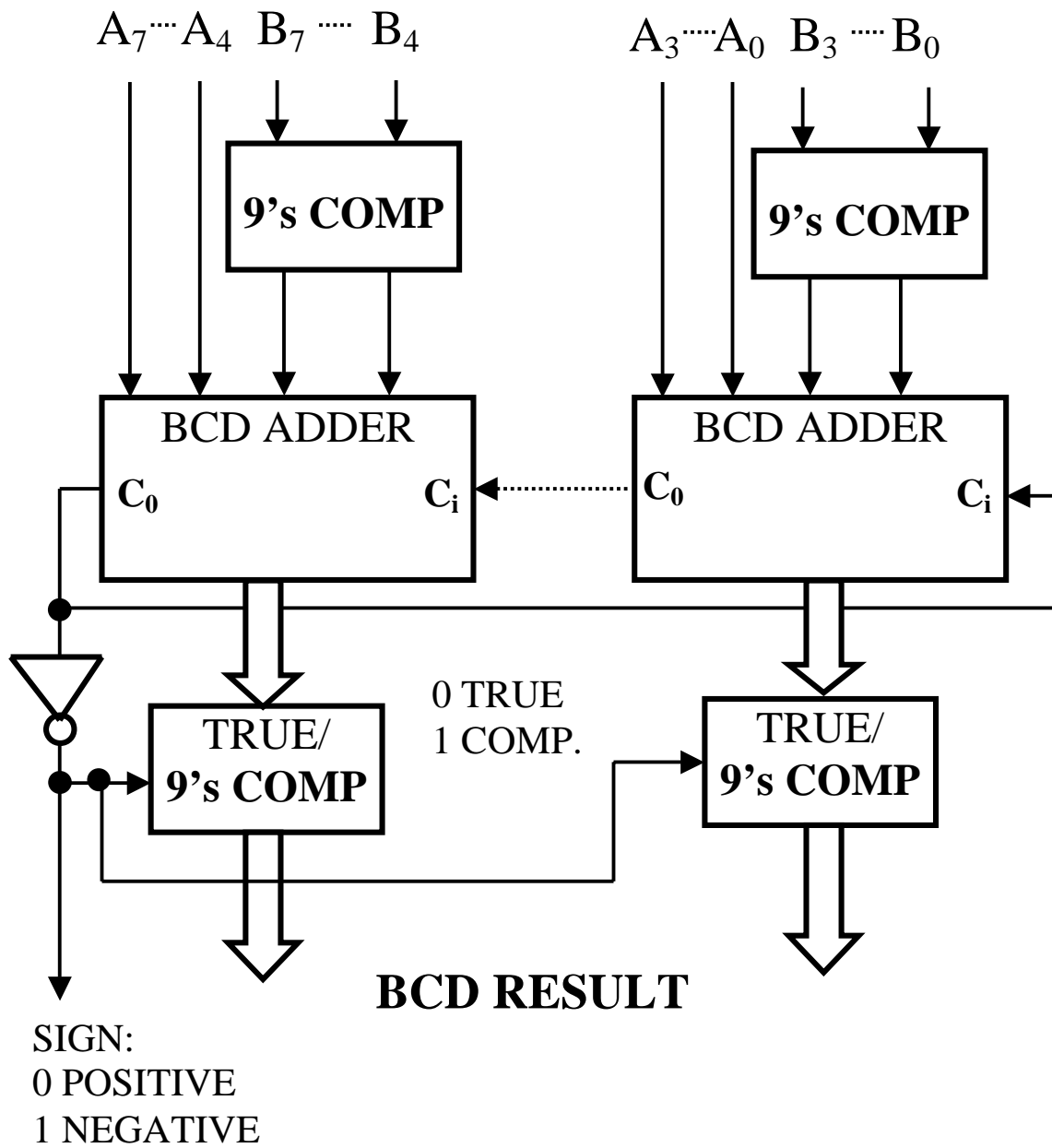

9's COMPLEMENT


**9's COMPLEMENT OF A NUMBER
= 9 – NUMBER**

**BUT SUBTRACTORS ARE NOT WIDELY
AVAILABLE >>> WE GENERATE THE
9's COMPLEMENT BY ADDING 1010 TO
THE INVERTED NUMBER**

BCD DIGIT	$\overline{\text{DIGIT}}$	$\overline{\text{DIGIT}} + 1010$ = 9's COMP $C_3 C_2 C_1 C_0$
0 0 0 0	1 1 1 1	1 0 0 1
0 0 0 1	1 1 1 0	1 0 0 0
0 0 1 0	1 1 0 1	0 1 1 1
0 0 1 1	1 1 0 0	0 1 1 0
0 1 0 0	1 0 1 1	0 1 0 1
0 1 0 1	1 0 1 0	0 1 0 0
0 1 1 0	1 0 0 1	0 0 1 1
0 1 1 1	1 0 0 0	0 0 1 0
1 0 0 0	0 1 1 1	0 0 0 1
1 0 0 1	0 1 1 0	0 0 0 0

WE IGNORE THE CARRY OUT

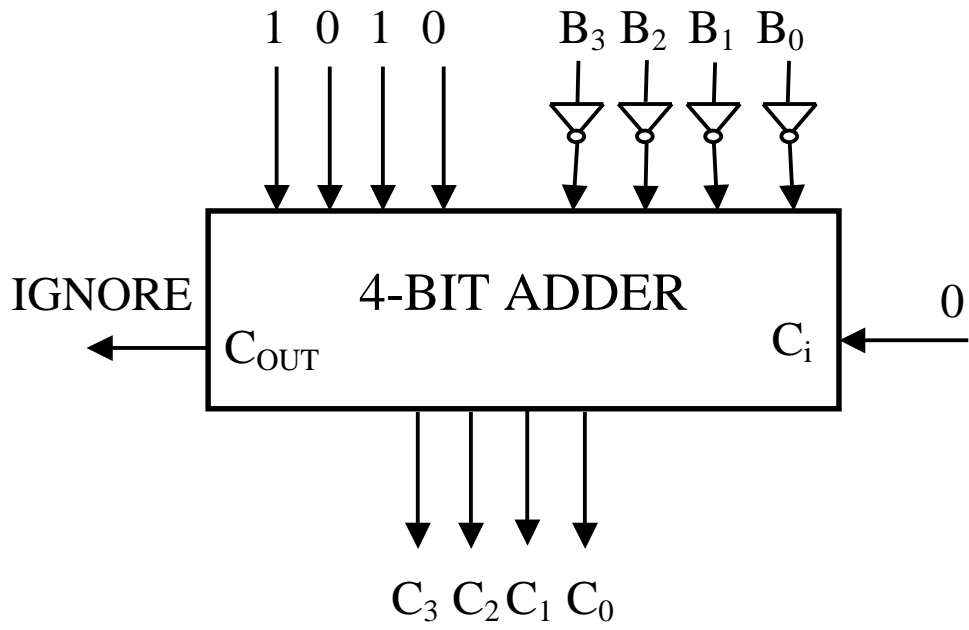EXERCISE: DESIGN A 9's COMPLEMENT GENERATOR FOR A BCD DIGIT:



OCTAL & HEXADECIMAL NUMBERS

TWO MORE NUMBER SYSTEMS

OCTAL >>> BASE 8 E.G. 3_8

HEXADECIMAL >>> BASE 16 E.G. 5_{16}

THE OCTAL NUMBER SYSTEM IS
COMPOSED OF 8 DIGITS:

0, 1, 2, 3, 4, 5, 6, 7

**TO COUNT ABOVE 7, WE BEGIN
ANOTHER COLUMN AND START
OVER:**

10, 11, 12, 13, 14, 15, 16, 17, 20, 21,...

**>>> COUNTING IN OCTAL IS SAME AS
COUNTING IN DECIMAL EXCEPT ANY
NUMBERS WITH 8 OR 9 WHICH ARE
OMITTED.**

THE HEXADECIMAL SYSTEM IS COMPOSED OF 16 DIGITS AND CHARACTERS. EACH HEXADECIMAL CHARACTER REPRESENTS a 4-BIT BINARY NUMBER

DECIMAL	OCTAL	HEXADECIMAL
0	0	0
1	1	1
2	2	2
3	3	3
4	4	4
5	5	5
6	6	6
7	7	7
8	10	8
9	11	9
10	12	A
11	13	B
12	14	C
13	15	D
14	16	E
15	17	F
16	20	10

17	21	11
18	22	12
19	23	13
20	24	14
⋮	⋮	⋮
24	30	18
⋮	⋮	⋮
32	40	20

DECIMAL >>> OCTAL

DIVIDE BY 8, GET REMAINDERS AND READ UP.

$$\begin{array}{r}
 123_{10} : 8 \\
 15 : 8 \quad 3 \quad \uparrow \\
 1 : 8 \quad 7 \quad \uparrow \text{ READ UP} \\
 0 \quad 1
 \end{array}$$

$$>>> 123_{10} = 173_8$$

$$\begin{array}{r} \text{(b)} \quad 100_{10} : 8 \\ 12 : 8 \quad 4 \\ \quad 1 : 8 \quad 4 \\ \quad \quad 0 \quad 1 \end{array} \begin{array}{c} \uparrow \\ \text{READ UP} \end{array}$$

$$\ggg 100_{10} = 144_8$$

OCTAL \ggg DECIMAL

MULTIPLY BY SUCCESSIVE POWERS OF 8

$$\begin{aligned} 173_8 &= 1 \times 8^2 + 7 \times 8^1 + 3 \times 8^0 \\ &= 64 + 56 + 3 = 123_{10} \end{aligned}$$

NOTE: WE BEGIN WITH **RIGHT-MOST POWER OF 8 AS 8^0**

DECIMAL \ggg HEXADECIMAL

DIVIDE BY 16, GET REMAINDERS AND READ UP

NOTE: REMAINDER = 13

\ggg USE CHARACTER **D**

E.G. $123_{10} : 16$
 $7 : 16$ $(11) \leftarrow \mathbf{B}$
 0 7

>>> $123_{10} = 7\mathbf{B}_{16}$

HEXADECIMAL >>> DECIMAL

MULTIPLY BY SUCCESSIVE POWERS OF 16

NOTE: WE CONVERT A CHARACTER TO ITS DECIMAL VALUE BEFORE WE MULTIPLY

E.G. $6\mathbf{A}_{16} = 6 \times 16^1 + \mathbf{A} \times 16^0$
 $= 6 \times 16^1 + 10 \times 16^0$
 $= 96 + 10 = \mathbf{106}_{10}$

SEQUENTIAL LOGIC

UNTIL NOW WE HAVE DEALT WITH COMBINATIONAL LOGIC – WHERE THE OUTPUT DEPENDED ON THE PRESENT COMBINATION OF INPUTS

IN SEQUENTIAL LOGIC THE OUTPUT DEPENDS ON THE PAST INPUTS AS WELL AS PRESENT INPUTS


E.G. MEMORY DEVICES USED TO REMEMBER PAST VALUES OF INPUTS

FLIP-FLOPS

DIGITAL MEMORIES, COUNTERS AND SHIFT REGISTERS ARE BASED ON THE FLIP-FLOP. THIS IS A DEVICE THAT CAN STORE 2 STATES 0 OR 1

R-S FLIP-FLOP

 THE BASIC RS [RRESET- SSET] FLIP-FLOP CONSISTS OF 2 NOR GATES WITH THE OUTPUTS CROSS-COUPLED TO THE INPUTS



R	S	Q	\bar{Q}	
0	0	NO CHANGE		
0	1	1	0	SET
1	0	0	1	RESET
1	1	NOT ALLOWED		

START WITH A KNOWN STATE

R = 0, S = 1 >>> Q = 1 SET

R = 1, S = 0 >>> Q = 0 RESET

WHEN $R=S=0$, Q AND \bar{Q} REMAIN AS THEY WERE BEFORE THE INPUT WAS CHANGED

$R=S=1$ IS NOT ALLOWED AS IT CAUSES $Q=\bar{Q}=0$ >>> THEY HAVE TO BE OPOSITE TO EACH OTHER

APPLICATION: MEMORY CELL

R	S	Q_N	\bar{Q}_N	Q_{N+1}	\bar{Q}_{N+1}
0	0	0	1	0	1
0	0	1	0	1	0


N = PREVIOUS STAGE (PAST)

N+1 = PRESENT STAGE

THE CIRCUIT IS SAID TO BE **BISTABLE**
>>> IT CAN ASSUME **TWO STABLE STATES.**

RS FLIP-FLOP USING NAND GATES

** TWO CROSS-COUPLED NAND GATES

 

S	R	Q	\bar{Q}
0	0	NOT ALLOWED	
0	1	1	0
1	0	0	1
1	1	NO CHANGE	


SET

RESET

ACTIVE LOW RS

THE RS FLIP-FLOP CAN BE USED TO ELLIMINATE “CONTACT BOUNCES” IN SWITCHES.

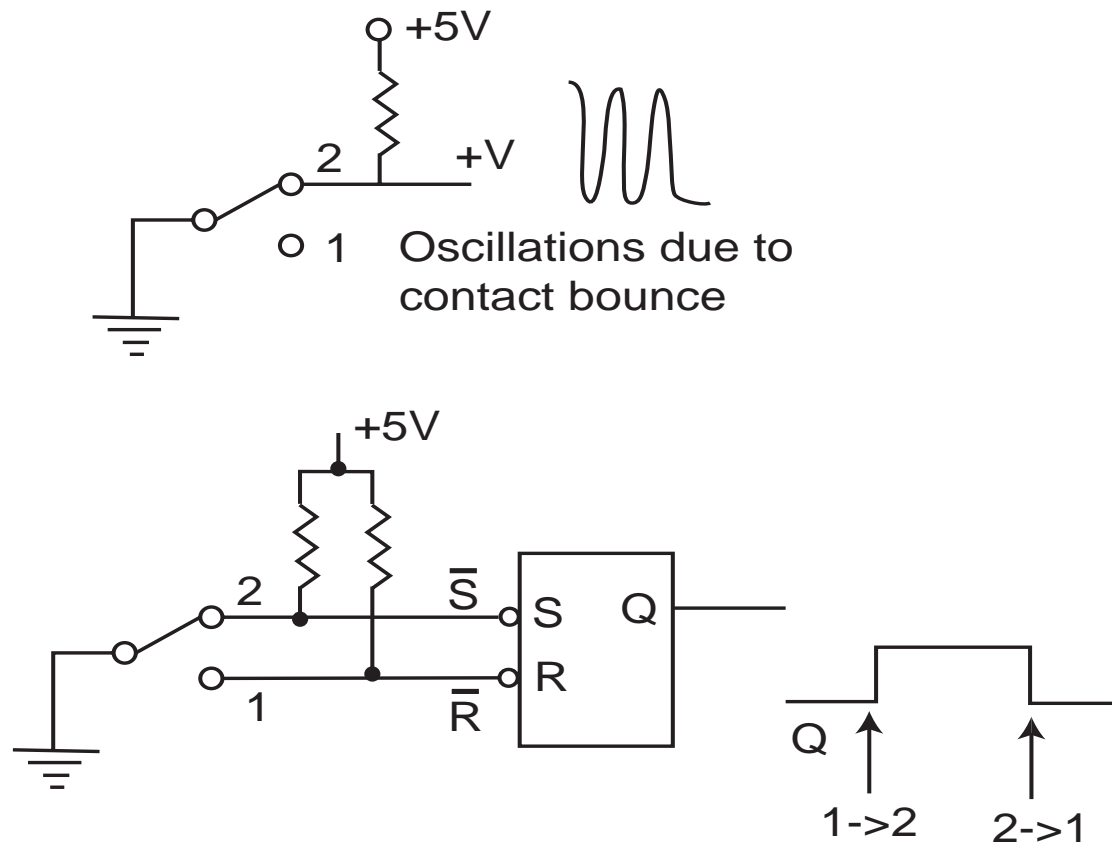ELECTRICAL CONTACTS OFTEN PROVIDE INPUT SIGNALS TO LOGIC SYSTEMS >>> THESE CONTACTS MAY BE A SOURCE OF NOISE DUE TO THEIR MECHANICAL PROPERTIES.




SWITCH MOVES FROM 1 TO 2 Q CHANGES FROM 0 TO 1 AS SOON AS THE FIRST CONTACT IS MADE (EVEN IF THE SWITCH BOUNCES Q STAYS AT 1)

WHEN THE SWITCH MOVES FROM 2 TO 1 Q CHANGES FROM 1 TO 0 AS SOON AS THE FIRST CONTACT IS MADE.

SYNCHRONOUS [CLOCKED] RS FLIP-FLOP

 **WE OFTEN NEED TO SET OR RESET A
FLIP-FLOP UNDER THE CONTROL OF
A CLOCK PULSE**



**REMEMBER: $S' = R' = 1$ NO OUTPUT
CHANGE**

WHEN CLOCK APPLIED


S_N	R_N	Q_n	$\overline{Q_n}$
→	→	→	→
FF			

S_N	R_N	Q_{n+1}	$\overline{Q_{n+1}}$
0	0	Q_n	$\overline{Q_n}$
0	1	0	1
1	0	1	0
1	1	NOT ALLOWED	

n = TIME BEFORE THE CLOCK PULSE

$n+1$ = TIME AFTER THE CLOCK PULSE


 
HERE THE FLIP-FLOP IS SET OR RESET UNDER THE CONTROL OF THE CLOCK PULSE



WHEN CLK IS AT “0” NO CHANGE IN OUTPUTS **IRRESPECTIVE** OF THE STATE OF **THE INPUTS (S,R)**.

D FLIP-FLOP

  D [**DELAY**] FLIP-FLOP IS A SIMPLE **EXTENSION** OF THE **CLOCKED RS** FLIP-FLOP WITH THE **D** INPUT CONNECTED TO THE “**SET**” INPUT AND $\overline{\mathbf{D}}$ CONNECTED TO THE “**RESET**” INPUT.



D	Q_{n+1}	$\overline{Q_{n+1}}$
0	0	1
1	1	0

D=1 >>> SET

D=0 >> RESET

ACTS AS 1-BIT DTORAGE ELEMENT

INPUT TRANSFERRED TO OUTPUT

>>>> CALLED A LATCH.


J-K FLIP-FLOP

J-K FLIP-FLOP ELIMINATES NON-DEFINED (NOT ALLOWED) STATE THAT OCCURRED IN THE RS FLIP-FLOP ($R=S=1$).

MOST VERSATILE AND WIDELY USED.


Q_n	J	K	Q_{n+1}	
0	0	0	0	NO CHANGE
0	0	1	0	RESET
0	1	0	1	SET
0	1	1	1	TOGGLE
1	0	0	1	NO CHANGE
1	0	1	0	RESET
1	1	0	1	SET
1	1	1	0	TOGGLE

WHEN CLOCK ACTIVE

 

**DIFFERS TO R-S BY USING
ADDITIONAL FEEDBACK**

WHEN CLOCK ACTIVE

 

J	K	Q_{n+1}	
0	0	Q_n	NO CHANGE
0	1	0	RESET
1	0	1	SET
1	1	$\overline{Q_n}$	TOGGLE

**SAME AS R-S FLIP-FLOP EXCEPT
WHEN $J=K=1$.**


E.G. $Q=0$ [$\bar{Q}=1$] >>> RESET
THEN CLOCK GOES FROM 0 \rightarrow 1

>>> $A \rightarrow 0$ >>> $Q=1$
 $B \rightarrow 1$ >>> $Q=1$
 >>> SET


MASTER SLAVE J-K FLIP-FLOP

 PROBLEM WITH J-K FLIP-FLOP >>>
OUTPUTS MAY CHANGE IF THE DATA
INPUTS [J, K, Q, \bar{Q}] CHANGE WHILE THE
CLOCK IS HIGH

>>> WE NEED TO MAKE SURE THAT Q
AND \bar{Q} DO NOT ASSUME THEIR NEW
VALUES UNTIL AFTER THE TRAILING
EDGE ON THE CLOCK PULSE i.e. WHEN
PULSE $\rightarrow 0$



 WE DO THIS BY USING A **MASTER-SLAVE** [M-S] FLIP-FLOP >>> **DIVIDE** THE FLIP-FLOP INTO **MASTER + SLAVE** FLIP-FLOP.



WHEN THE CLOCK PULSE IS **HIGH** THE J-K INPUTS ARE APPLIED TO THE **MASTER FLIP-FLOP** AND THE **SLAVE INPUT** IS NOT AFFECTED ($\overline{\text{CLK}}=0$)

WHEN THE CLOCK PULSE **FALLS TO ZERO**, THE **DATA FROM THE MASTER** IS APPLIED TO THE **SLAVE INPUTS** AND THE OUTPUTS **Q** AND **Q-bar** GET THEIR NEW VALUES.

ANOTHER RESTRICTION: THE INPUTS J AND K DO NOT CHANGE WHILE CLK=1

A **R-S** MASTER SLAVE FLIP-FLOP MAY ALSO BE CONSTRUCTED IN A SIMILAR FASHION, THE ONLY DIFFERENCE IS THAT WHEN **THE TWO INPUTS J=K=1** THE OUTPUT **Q** CHANGES IS STATE ON RECEIPT OF THE CLOCK PULSE i.e. THE FLIP-FLOP **TOGGLES**.

J	K	Q_{n+1}	
0	0	Q_n	UNCAHGED
0	1	0	RESET
1	0	1	SET
1	1	$\overline{Q_n}$	TOGGLE

DIFFERENT APPROACH:

WE WILL NOW LOOK AT THE J-K FLIP FLOP IN A SLIGHTLY DIFFERENT WAY

IF **$Q_n = 0$ AND $J = 0$ >>> $Q_{n+1} = 0$**
REGARDLESS OF **K**

IF **$Q_n = 0$ AND $J = 1$ >>> $Q_{n+1} = 1$**
REGARDLESS OF **K**

**IF $Q_n = 1$ AND $K = 0$ \gggg $Q_{n+1} = 1$
REGARDLESS OF J**

**IF $Q_n = 1$ AND $K = 1$ \gggg $Q_{n+1} = 0$
REGARDLESS OF J**

J	K	Q_n	Q_{n+1}	$\overline{Q_{n+1}}$
0	X	0	0	1
1	X	0	1	0
X	1	1	0	1
X	0	1	1	0

**“X” → DEFINES A DON’T CARE TERM
→ USEFUL IN DESIGNING LOGIC
SYSTEMS WITH J-K FLIP FLOPS**


**THE MASTER-SLAVE FLIP-FLOPS ARE
SYNCHRONOUS DEVICES \gggg THE
OUTPUT CHANGES STATE AT A
SPECIFIED POINT ON A CLOCK
INPUT.**

J-K FLIP-FLOP WITH ASYNCHRONOUS SET AND RESET INPUTS

SEPARATE “SET” AND “RESET” INPUTS MAY BE ADDED TO THE J-K FLIP FLOP.

THESE SET & RESET INPUTS $[\bar{S}, \bar{R}]$ OVER-RIDE THE J,K INPUTS AND ARE ASYNCHRONOUS [i.e. OVER-RIDE THE CLOCK ALSO].

 NOTE: WHEN $\bar{S} = \bar{R} = 1 \gg \gg$ WE HAVE NORMAL FLIP-FLOP OPERATION



TRUTH TABLE:

\bar{S}	\bar{R}	J	K	Q_{n+1}	
0	0	X	X	NOT ALLOWED	
0	1	X	X	1	
1	0	X	X	0	
1	1	0	0	Q_n	NORMAL OPERATION
1	1	0	1	0	
1	1	1	0	1	
1	1	1	1	\bar{Q}_n	

FLIP-FLOP APPLICATIONS


REGISTERS:

GROUPS OF FLIP-FLOPS ARRANGED TO PROVIDE DATA STORAGE FOR SEVERAL DATA BITS.

 1. DATA REGISTER

A J-K FLIP-FLOP CAN BE USED AS A 1-BIT MEMORY [D FLIP-FLOP] BY APPLYING THE BIT TO BE STORED [D] TO J AND ITS INVERSE [\bar{D}] TO K. AN “n” BIT BINARY WORD CAN BE STORED BY “n” SUCH FLIP-FLOPS >>>> CALLED A n-BIT REGISTER.

PARALLEL DATA STORAGE, i.e. SEVERAL BITS ON PARALLEL LINES STORED SIMULTANEOUSLY.




DATA BITS ($D_3 - D_0$) ARE STORED ON THE RECEIPT OF THE CLOCK PULSE.

2. SHIFT REGISTER

SERIAL DATA TRANSFER [i.e. ONE BIT AT A TIME], A WORD OF N-BITS READ INTO N-FLIP-FLOP SHIFT REGISTER

THE FIRST FLIP-FLOP HOLDS THE WORD'S MSB AND IS CONNECTED AS A D FLIP-FLOP.

E.G. 4 –BIT SHIFT REGISTER

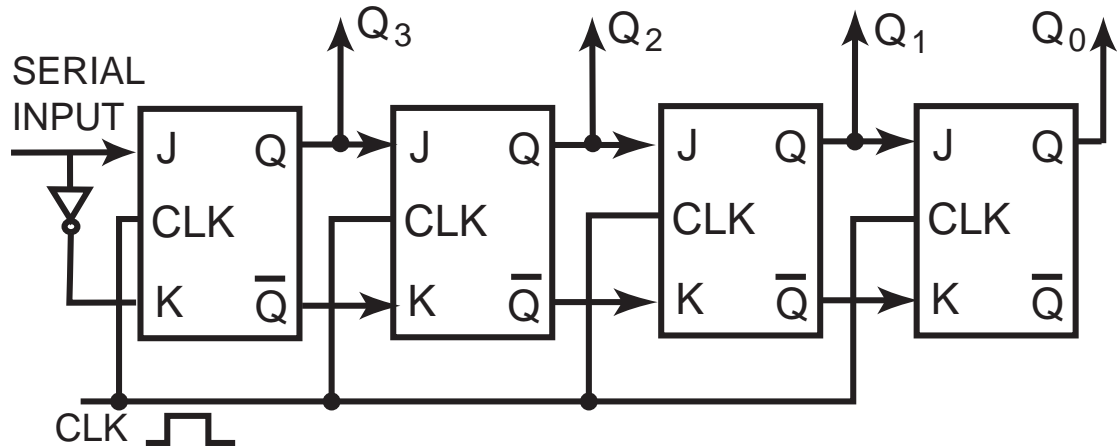

Q3 = MSB

REMEMBER:

J	K	Q_{n+1}
0	1	0
1	0	1

OUTPUT FOLLOWS **J**-INPUT WHEN **J = \bar{K}**

>>> SHIFT OCCURS WHEN CLOCK APPLIED.

SHIFT REGISTER OPERATION:

LSB OF SERIAL DATA IS APPLIED TO THE SERIAL INPUT [J_3]. THE CLOCK PULSE IS APPLIED AND LSB GOES INTO Q_3 [= J_2]. THE NEXT LSB IS THEN APPLIED TO J_3 AND AFTER A CLOCK PULSE IT IS STORED IN Q_3 , WHILE AT THE SAME TIME THE LSB IS SHIFTED INTO Q_2 .

AFTER 4 CLOCK PULSES THE SERIAL DATA IS STORED IN THE SHIFT REGISTER.


E.G. STORE THE WORD: 0 1 0 1

CLK	SERIAL INPUT	Q_3	Q_2	Q_1	Q_0
1	1 →	1	0	0	0
2	0 →	0	1	0	0
3	1 →	1	0	1	0
4	0 →	0	1	0	1

ASSUME THE STORED WORD IS INITIALLY **0 0 0 0**.

 3. SHIFT REGISTERS WITH PARALLEL INPUTS **[PARALLEL TO SERIAL CONVERTER]**

- LOAD BITS IN PARALLEL FORM AND SHIFT THEM IN SERIAL FORM.
- DATA IS LOADED BY APPLYING SIGNALS TO ASYNCHRONOUS SET/RESET INPUTS OF THE J-K FLIP-FLOP.



PARALLEL DATA IS LOADED BY APPLYING A CLOCK PULSE TO “PARALLEL LOAD” SIGNAL.

WHEN “PARALLEL LOAD” IS LOW THE CIRCUIT OPERATES AS A NORMAL SHIFT REGISTER [$\overline{S} = \overline{R} = 1$]

WHEN “PARALLEL LOAD” IS HIGH THEN PARALLEL DATA IS LOADED ASYNCHRONOUSLY [INDEPENDENT OF THE CLOCK] AND SHIFTED OUT SYNCHRONOUSLY.

4. RIGHT-LEFT SHIFT REGISTER

SHIFT REGISTERS CAN ALSO BE USED TO TRANSFER DATA FROM RIGHT TO LEFT, SHIFT LEFT, BY CONNECTING THE OUTPUT OF A FLIP-FLOP BACK TO THE INPUT OF THE FLIP-FLOP ON ITS LEFT

A SHIFT FROM LEFT TO RIGHT, SHIFT RIGHT, CAN BE CARRIED OUT DURING NORMAL OPERATION OF THE SHIFT REGISTER.

A SHIFT RIGHT AND SHIFT LEFT REGISTER CAN BE COMBINED BY SUITABLE GATING AND CONTROL SIGNALS.

**NOTE $\bar{R}/L \gg \gg \bar{R}/L = 0 \gg \gg$ SHIFT RIGHT
 $\bar{R}/L = 1 \gg \gg$ SHIFT LEFT**

